

Project Manual

Simulation Steering Wheel

ESCE 2010 - Fall 2025

August Bernberg

October 8, 2025

Project Resources

LTSpice Simulation File:

Github Link to .asc File

Contents

1	Description	3
1.1	Complete Schematic and Block Diagram	3
1.2	High-Level Description of Operation and Intended Application	3
1.3	Description of Related Pre-Existing Applications	3
2	Operation and Design	5
2.1	Input Block	5
2.1.1	Schematic	5
2.1.2	Design Equation	5
2.1.3	Input/Output Plot	5
3	MS1 Building Block 1	6
3.1	Schematic	6
3.2	Design Equation	6
3.3	Discussion of Component Choices	6
3.4	Input/Output Plot	8
3.5	Output Block	9
3.5.1	Schematic	9
3.5.2	Design Equation	9
3.5.3	Input/Output Plot	9
4	Integration and Optimization	10
4.1	MS1	10
5	Operating Conditions	11
5.1	MS1	11
5.1.1	Limitations and Faults	11
5.1.2	Tradeoffs Present in the Design	11
5.1.3	Circuit Improvements	11
6	ABET 3.2 Engineering Design Considerations	12
7	References	13

1 Description

1.1 Complete Schematic and Block Diagram



A large, pixelated, black text graphic that reads "Download".

Figure 1: Complete circuit schematic - ALL major components must be clearly labeled



A large, pixelated, black text graphic that reads "Download".

Figure 2: Block diagram showing functional relationships between stages

1.2 High-Level Description of Operation and Intended Application

This project focuses on the design and fabrication of a custom simulation steering wheel, integrating load cells, buttons, and a servo to create a realistic driving experience for the user. The load cells measure precise grip force which is translated into throttle or braking; the buttons are timely triggered for insim actions; and the servo motor's rotational data is measured for steering functionality. All sensor data is then read and translated by the HID(Human Interface Device) format and relayed to a computer via a microcontroller - the microcontroller's only purpose is to read, not manipulate external data - which allows for seamless communication with a simulation software/application.

1.3 Description of Related Pre-Existing Applications

There are numerous existing sim wheel options from manufacturers such as LogitechG, Thrustmaster, and others. Entry-level models typically start around \$100, with midrange units costing up to \$300, and high-end versions—featuring force feedback, F1-style layouts, and other advanced features—reaching significantly higher prices. In contrast, this project aims to deliver similar functionality at a fraction of the cost, while maintaining high precision, simplicity, and ease of construction. However, unlike other commercial simulation wheels that rely heavily on microcon-

trollers to handle sensor inputs, this design focuses on hardware solutions while using as little power from a microcontroller, besides HID formatting, which has a combination of pros and cons.

2 Operation and Design

2.1 Input Block

2.1.1 Schematic



A large, bold, black text "Download" is centered on the page, serving as a placeholder for Figure 3.

Figure 3: Input block schematic with ALL components labeled

2.1.2 Design Equation

$$V_{out} = f(V_{in}) \quad (1)$$

where all variables are defined here or in the schematic.

2.1.3 Input/Output Plot



A large, bold, black text "Download" is centered on the page, serving as a placeholder for Figure 4.

Figure 4: I/O characteristic - from measurement, simulation, or datasheet (cite source!)

3 MS1 Building Block 1

3.1 Schematic

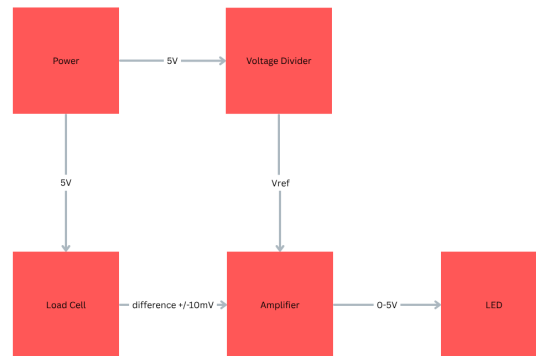


Figure 5: Building Block 1.1

3.2 Design Equation

Load Cell Output: *manufactures provide no internal resistances of wheatstone bridge besides output voltage*

$$V_{out} = \pm 10mV$$

Amplifier Gain:

$$G_m = 1 + \frac{49.4k\Omega}{R_G}$$

Voltage Divider:

$$V_{out} = V_{in} \times \frac{R_1}{R_1 + R_2}$$

Defined variables:

- G_m = gain multiplier
- R_G = resistor gain
- V_{out} = output to amplifier reference pin(6 recieving 2)
- R_1 & R_2 = resistors for voltage divider to get 2.5V output

3.3 Discussion of Component Choices

The loadcell has a 10mV output according to the manufacture(there is no information regarding the internal wheatstone bridge so cant provide a schematic for that). This means to get an LED lighting output, there needs to be a gain to 5V, which is approximately 500x multiplier. However,

an input via a voltage divider supplies a baseline 2.5 volts, meaning there is only a required 50% gain, or 250x. Given the manufacture's gain of their AD8226 amp, it only requires a ~ 200 ohm resistor to reach my threshold.

3.4 Input/Output Plot

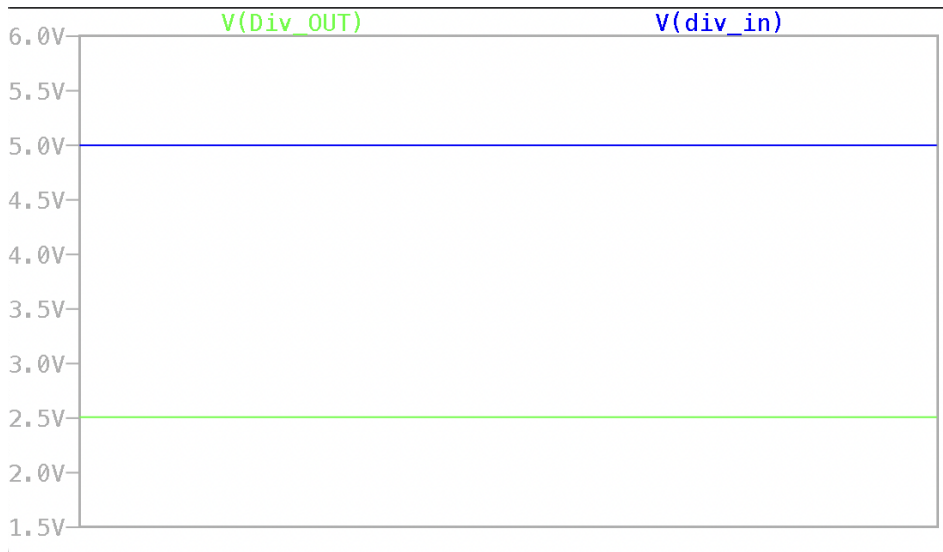


Figure 6: Voltage Divider

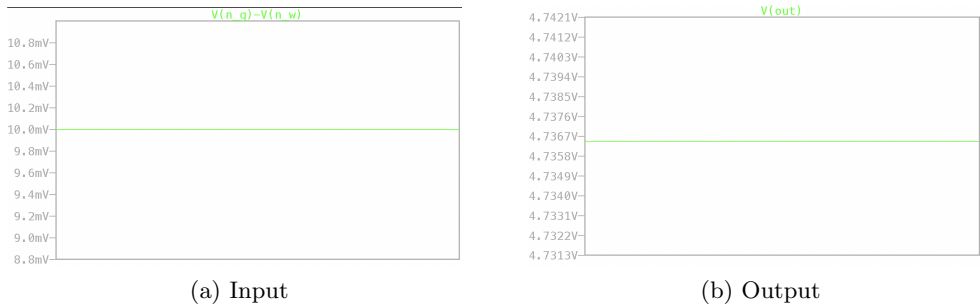


Figure 7: Amplifier

3.5 Output Block

3.5.1 Schematic

Download

Figure 8: Input block schematic with ALL components labeled

3.5.2 Design Equation

$$V_{out} = f(V_{in}) \quad (2)$$

where all variables are defined here or in the schematic.

3.5.3 Input/Output Plot

Download

Figure 9: I/O characteristic - from measurement, simulation, or datasheet (cite source!)

4 Integration and Optimization

4.1 MS1

5 Operating Conditions

5.1 MS1

5.1.1 Limitations and Faults

A major limitation for this milestone is lack of complete data. The adafruit manufacturing team has provided poor documentation and schematics relating to their loadcell - only providing a Mandarin transcribed diagram with limited and inaccurate information(i.e. states range is 1-10kg but the one it is referencing is supposedly caps at 20kg load). Besides that

5.1.2 Tradeoffs Present in the Design

5.1.3 Circuit Improvements

6 ABET 3.2 Engineering Design Considerations

...

7 References

References

Appendix